

**University of Miami**  
**EEN 414 Computer Organization and Design**  
**EXPERIMENT #4. Divider**

**Submitted by:** Brandon Rubio, Isabela Bandrich, Rainier Young, Nikeem Dunkelly-Allen

**On:** 10/28/22

**to :** Dr. Onur Tigli

**Objective**

In this experiment, you are required to apply datapath and control unit design techniques in Verilog HDL to design and optimize a division algorithm. Coding, verification, simulation, synthesis and timing analysis will be carried out using Xilinx ISE tools. Verified designs will be implemented on Digilent's NEXYS-4 FPGA boards for demonstration of correct operation.

**Verilog HDL and Testbench Code**

**MAIN CODE:**

**Counter:**

```
always @(posedge clk)
begin
    if(clr)
        count <= 0;
    else
        begin
            if(increment)
                count <= count + 1'b1;
            else
                count <= count;
        end
    end
endmodule
```

**Controller:**

```

33     begin
34         if(reset) state<=S0;
35     else begin
36         case(state)
37             S0: state<=S1;
38             S1: begin
39                 if(sub_count) state<=S3;
40                 else state<=S2;
41             end
42             S2: begin
43                 if(counter==nBit-1) state<=S5;
44                 else state<=S4;
45             end
46             S3: begin
47                 if(counter==nBit-1) state<=S5;
48                 else state<=S4;
49             end
50             S4: state<=S1;
51             S5: state<=S5;
52             default: state<=S0;
53         endcase
54     end
55 end

```

```

70     end
71     else if(state==S2) begin
72         R_Load<=1'b0;
73         R_ShiftLeft<=1'b0;
74         Q_ShiftLeft<=1'b1;
75     end
76     else if(state==S3) begin
77         R_Load<=1'b1;
78         R_ShiftLeft<=1'b0;
79         Q_ShiftLeft<=1'b1;
80     end
81     else if(state==S4) begin
82         A_ShiftLeft<=1'b1;
83         R_Load<=1'b0;
84         R_ShiftLeft<=1'b0;
85         Q_ShiftLeft<=1'b0;
86     end
87     else if(state==S5) begin
88         R_Load<=1'b0;
89         Q_ShiftLeft<=1'b0;
90     end
91     end
92 endmodule

```

**Datapath:**

```

30     output reg [nBit-1:0] Q
31     );
32     parameter nBit = 16;
33     wire [3:0] count;
34     wire [nBit-1:0] A_output, B_output, R_output, Q_output;
35     wire [nBit-1:0] Subtract;
36     wire [nBit-1:0] is_empty;
37     assign is_empty = 0;
38     |
39     Counter bit_count(A_ShiftLeft, clk, reset, count);
40     Shift_Registers #(nBit) ra(A, clk, AB_Load, 1'b0, A_ShiftLeft, 1'b0, 1'b0, A_output);
41     Shift_Registers #(nBit) rb(B, clk, AB_Load, 1'b0, 1'b0, 1'b0, 1'b0, B_output);
42     Shift_Registers #(nBit) rr(Subtract, clk, R_Load, AB_Load, R_ShiftLeft, 1'b0, A_output[nBit-1], R_output);
43     N_Subtractor #(nBit) sub(R_output, B_output, Subtract, sub_count);
44     Shift_Registers #(nBit) rq(is_empty, clk, 1'b0, AB_Load, Q_ShiftLeft, 1'b0, R_Load, Q_output);
45
46     assign shift_count = count;

```

```

52         Q<=Q_output;
53     end
54     else begin
55         R<=1'b0;
56         Q<=1'b0;
57     end
58 end
59
60 endmodule

```

### Divider:

```

27     wire [nBit-1:0] R_output;
28     wire [nBit-1:0] Q_output;
29     wire AB_Load, A_ShiftLeft;
30     wire R_Load, R_ShiftLeft;
31     wire Q_ShiftLeft;
32     wire sub_count;
33     wire [3:0] counter;
34
35     Controller #(nBit) cont(sub_count, clk, reset, counter, AB_Load, A_ShiftLeft, R_Load, R_ShiftLeft, Q_ShiftLeft);
36     Datapath #(nBit) data(A, B, clk, reset, AB_Load, A_ShiftLeft, R_Load, R_ShiftLeft, Q_ShiftLeft, counter, sub_count, R_output, Q_output);
37     assign R = R_output;
38     assign Q = Q_output;
39
40 endmodule

```

### Shift Registers:

```

28
29     always @(negedge clk)
30     begin
31         if(clr) Output<=1'b0;
32         else begin
33             if(load) Output<=Input;
34             else if(Shift_Left) Output<={Output[nBit-2:0], Shift_In};
35             else if(Shift_Right) Output<={Shift_In, Output[nBit-1:1]};
36             else Output<=Output;
37         end
38     end
39 endmodule

```

**Half Adder:**

```

23     output S, Cout
24 );
25     xor(S, A, B);
26     and(Cout, A, B);
27
28 endmodule

```

**Full Adder:**

```

24 );
25     wire D, E, F;
26     Half_Adder hal(A, B, D, E);
27     Half_Adder ha2(Cin, D, S, F);
28     or(Cout, E, F);
29
30 endmodule

```

### N Subtractor:

```
27     wire [nBit-1:0] Bin, B;
28     assign Bin = ~C + 1'b1;
29
30     genvar i;
31     generate
32         for(i=0;i<=nBit-1;i=i+1)
33             begin: generate_subtractor
34                 if(i==0) Half_Adder ha(A[0], Bin[0], D[0], B[0]);
35                 else Full_Adder fa(A[i], Bin[i], B[i-1], D[i], B[i]);
36             end
37             assign Bout = B[nBit-1];
38     endgenerate
39
40 endmodule
```

### Seven Segment Decoder:

```

31         4'h2 : tmp = 8'b01001001;
32         4'h3 : tmp = 8'b01100001;
33         4'h4 : tmp = 8'b00110011;
34         4'h5 : tmp = 8'b00100101;
35         4'h6 : tmp = 8'b00000101;
36         4'h7 : tmp = 8'b11110001;
37         4'h8 : tmp = 8'b00000001;
38         4'h9 : tmp = 8'b00100001;
39         4'hA : tmp = 8'b00010001;
40         4'hB : tmp = 8'b00000111;
41         4'hC : tmp = 8'b10001101;
42         4'hD : tmp = 8'b01000011;
43         4'hE : tmp = 8'b00001101;
44         4'hF : tmp = 8'b00011101;
45         default : tmp = 8'b01111111;
46     endcase
47 end
48 assign sev_seg_leds[7:0] = tmp;
49 endmodule

```

### Seven Segment Display with Clock:

```

30     assign led_disable = 4'b1111;
31
32     always @(posedge clk or posedge reset)
33     begin
34         if(reset) begin
35             sel<=3'b000;
36             led_enable<=4'b1111;
37         end
38         else begin
39             sel[2]<=sel[1]&sel[0];
40             sel[1]<=sel[1]^sel[0];
41             sel[0]<=~sel[0];
42             if(sel==3'b001) begin
43                 led_enable<=4'b0111;
44                 bus<=num_1;
45             end

```

```

51             bus<=num_3;
52         end
53         else if(sel==3'b100) begin
54             led_enable<=4'b1110;
55             bus<=num_4;
56         end
57     end
58 end
59 end
60
61 Sev_Seg_Decoder dec1(bus, sev_seg_leds);
62
63 endmodule

```

**Seven Segment Display with Clock (Top Module):**



```

28
29     reg [14:0] clk_div;
30
31     Divider #(8) d(num_1, num_2, clk_slw, reset, num_3, num_4);
32     Sev_Seq_with_Clk dd(num_3[7:4], num_3[3:0], num_4[7:4], num_4[3:0], clk_div[14], reset, sev_seq_leds, led_disable, led_enable);
33     ip_clk_div clk_3N(clk_main, clk_slw);
34
35     always @(posedge clk_slw)
36     begin
37         if(reset) clk_div <= 15'd0;
38         else clk_div <= clk_div + 15'd1;
39     end
40
41 endmodule

```

**TESTBENCH:**

**tb\_Controller:**

```

35     wire A_ShiftLeft;
36     wire R_Load;
37     wire R_ShiftLeft;
38     wire Q_ShiftLeft;
39
40     // Instantiate the Unit Under Test (UUT)
41     Controller uut (
42         .sub_count(sub_count),
43         .clk(clk),
44         .reset(reset),
45         .counter(counter),
46         .AB_Load(AB_Load),
47         .A_ShiftLeft(A_ShiftLeft),
48         .R_Load(R_Load),
49         .R_ShiftLeft(R_ShiftLeft),
50         .Q_ShiftLeft(Q_ShiftLeft)
51     );

```

```

55     end
56
57     initial begin //reset
58         reset = 1'b1; //S0 and S1
59         #10;
60         reset = 1'b0;
61         #10;
62     end

```


```
73
74     reset = 1'b1; //S0 and S1
75     #10;
76     reset = 1'b0;
77     #10;
78
79     #10; //S3
80     sub_count = 1;
81     counter = 0;
82     #20;
83
84     sub_count = 1; //S4
85     counter = 0;
86     #20;
87 end
88
89 endmodule
```

**tb\_Divider:**

```
34     wire [15:0] R;
35     wire [15:0] Q;
36
37     // Instantiate the Unit Under Test (UUT)
38     Divider uut (
39         .A(A),
40         .B(B),
41         .clk(clk),
42         .reset(reset),
43         .R(R),
44         .Q(Q)
45     );
46     initial begin //clock
47         clk = 1'b0;
48         forever #1 clk = ~clk;
49     end
```

```
58  
59     B = 20;  
60     #200;  
61  
62     reset = 1'b1;  
63     #10;  
64     reset = 1'b0;  
65  
66     A = 55;  
67     B = 7;  
68     #200;  
69     end  
70  
71 endmodule
```

**ASM chart:**

 

State/Signal

S<sub>0</sub>: AB\_load\_QR\_clr = 1  
 A\_sl = 0  
 R\_load\_Q\_shiftln = 0  
 R\_sl = 0  
 Q\_sl = 0

S<sub>1</sub>: AB\_load\_QR\_clr = 0  
 A\_sl = 0  
 R\_sl = 1

S<sub>2</sub>: R\_load\_Q\_shiftln = 0  
 A\_sl = 0  
 Q\_sl = 1

S<sub>3</sub>: R\_load\_Q\_shiftln = 1  
 R\_sl = 0  
 Q\_sl = 1


S<sub>4</sub>: A\_sl = 1  
 R\_load\_Q\_shiftln = 0  
 R\_sl = 0  
 Q\_sl = 0

S<sub>5</sub>: R\_load\_Q\_shiftln = 0  
 Q\_sl = 0

## Simulation Results

Controller:



(State S0)

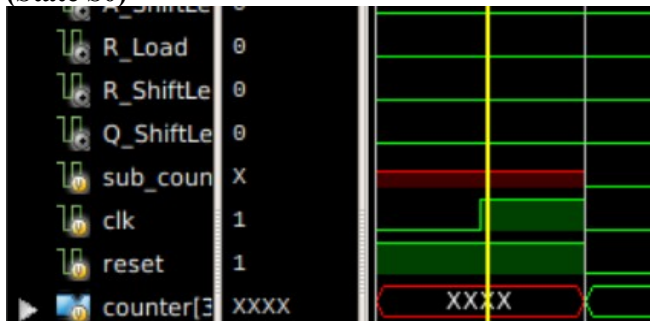


(State S1)




(State S2)

  

(State S3)

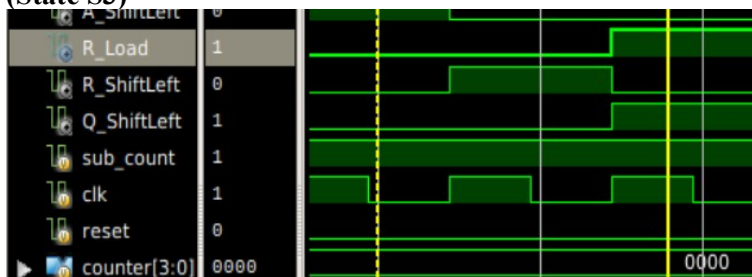

(State S4)

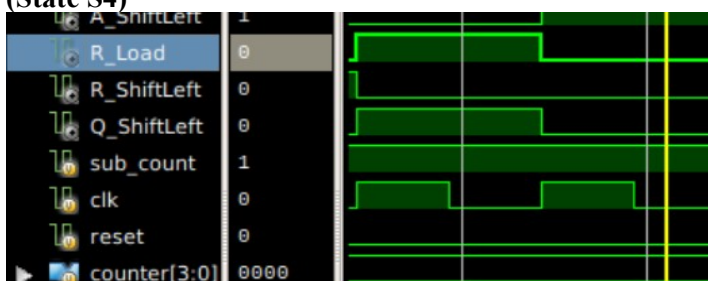


(State S5)




Divider:


(Resetting)

 

(Dividing 100 by 20)

 

(Dividing 55 by 7)

 

Pad2pad timing constraints




				Slack	Achievable	Errors	Score
1	Yes	<a href="#">Autotimespec constraint for clock net clk_BUFGP</a>	SETUP HOLD	0.178ns	8.678ns	0	0

**Device Utilization Summary**

**Divider:**



Number of Slice Registers	133	63400	0%
Number of Slice LUTs	79	165	47%
Number of fully used LUT-FF pairs	66	170	38%
Number of bonded IOBs	1	32	3%
Number of BUFG/BUFGCTRLs			

 



**RTL Schematic and Technology Schematic**

**Divider:**

**(RTL Schematic)**

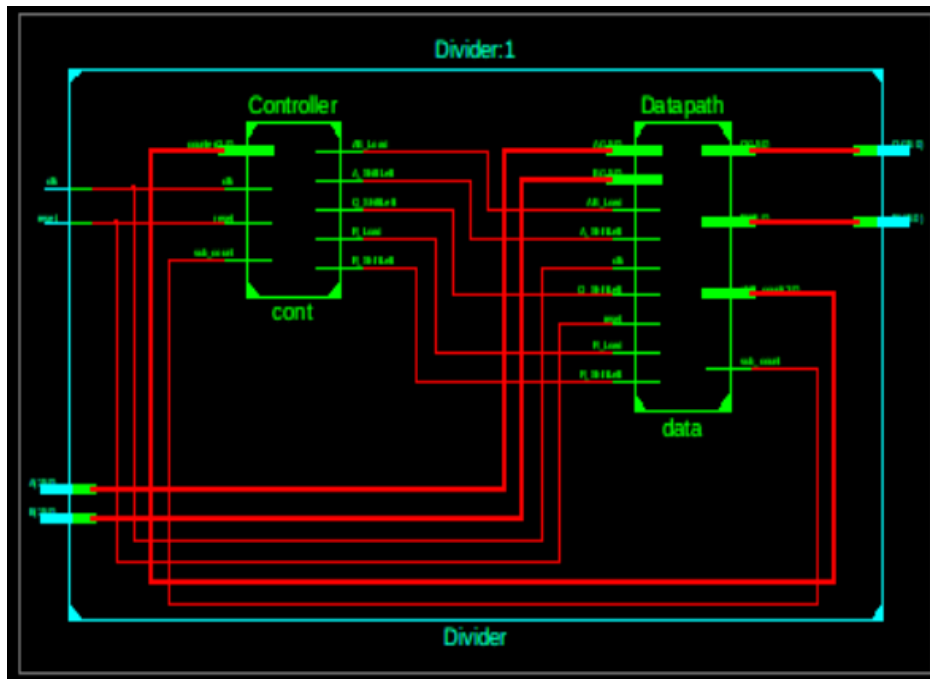 

(Technology Schematic)

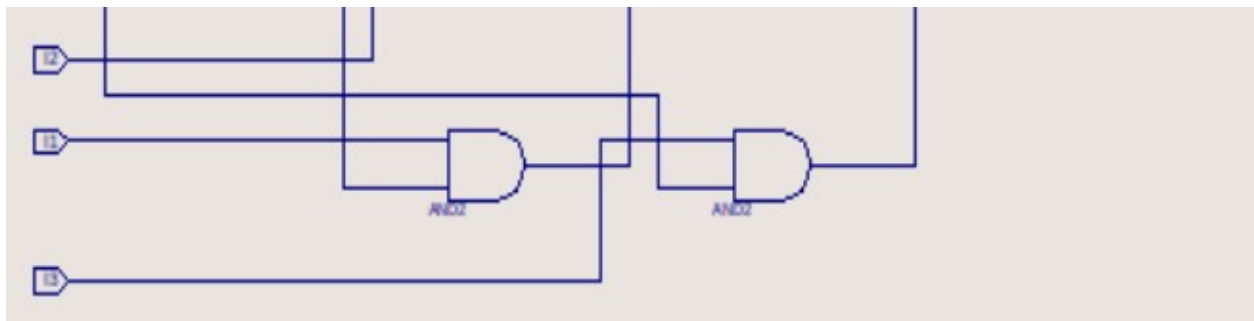 

### **Post Place and Route Static Timing**

INFO:Timing:2752 - To get complete path coverage, use the unconstrained paths option. All paths that are not constrained will be reported in the unconstrained paths section(s) of the report.

INFO:Timing:3339 - The clock-to-out numbers in this timing report are based on a 50 Ohm transmission line loading model. For the details of this model, and for more information on accounting for different loading conditions, please see the device datasheet.

A<3>	-0.468(F)	FAST	3.254(F)	SLOW	clk_BUFDP	0.000
A<4>	-0.574(F)	FAST	3.427(F)	SLOW	clk_BUFDP	0.000
A<5>	-0.607(F)	FAST	3.535(F)	SLOW	clk_BUFDP	0.000
A<6>	-0.447(F)	FAST	3.238(F)	SLOW	clk_BUFDP	0.000
A<7>	-0.450(F)	FAST	3.253(F)	SLOW	clk_BUFDP	0.000
A<8>	-0.484(F)	FAST	3.241(F)	SLOW	clk_BUFDP	0.000
A<9>	-0.424(F)	FAST	3.144(F)	SLOW	clk_BUFDP	0.000
A<10>	-0.590(F)	FAST	3.455(F)	SLOW	clk_BUFDP	0.000
A<11>	-0.471(F)	FAST	3.274(F)	SLOW	clk_BUFDP	0.000
A<12>	-0.031(F)	FAST	2.513(F)	SLOW	clk_BUFDP	0.000
A<13>	-0.043(F)	FAST	2.531(F)	SLOW	clk_BUFDP	0.000
A<14>	-0.311(F)	FAST	3.050(F)	SLOW	clk_BUFDP	0.000
A<15>	-0.242(F)	FAST	2.927(F)	SLOW	clk_BUFDP	0.000
B<0>	-0.216(F)	FAST	2.789(F)	SLOW	clk_BUFDP	0.000
B<1>	-0.102(F)	FAST	2.560(F)	SLOW	clk_BUFDP	0.000
B<2>	-0.166(F)	FAST	2.672(F)	SLOW	clk_BUFDP	0.000
B<3>	-0.074(F)	FAST	2.654(F)	SLOW	clk_BUFDP	0.000
B<4>	-0.283(F)	FAST	2.962(F)	SLOW	clk_BUFDP	0.000
B<5>	0.033(F)	FAST	2.471(F)	SLOW	clk_BUFDP	0.000
B<6>	-0.389(F)	FAST	3.139(F)	SLOW	clk_BUFDP	0.000
B<7>	-0.367(F)	FAST	3.008(F)	SLOW	clk_BUFDP	0.000

B<11>	-0.509(F)	FAST	3.337(F)	SLOW	clk_BUFDP	0.000
B<12>	-0.378(F)	FAST	3.067(F)	SLOW	clk_BUFDP	0.000
B<13>	-0.516(F)	FAST	3.318(F)	SLOW	clk_BUFDP	0.000
B<14>	-0.426(F)	FAST	3.171(F)	SLOW	clk_BUFDP	0.000
B<15>	-0.448(F)	FAST	3.231(F)	SLOW	clk_BUFDP	0.000
reset	-0.025(R)	FAST	2.648(R)	SLOW	clk_BUFDP	0.000

Q<9>	10.155(R)	SLOW	3.323(R)	FAST	clk_BUFGP	0.000
Q<10>	10.145(R)	SLOW	3.324(R)	FAST	clk_BUFGP	0.000
Q<11>	10.372(R)	SLOW	3.405(R)	FAST	clk_BUFGP	0.000
Q<12>	10.251(R)	SLOW	3.385(R)	FAST	clk_BUFGP	0.000
Q<13>	10.242(R)	SLOW	3.369(R)	FAST	clk_BUFGP	0.000
Q<14>	10.261(R)	SLOW	3.387(R)	FAST	clk_BUFGP	0.000
Q<15>	10.409(R)	SLOW	3.418(R)	FAST	clk_BUFGP	0.000
R<0>	0.028(R)	SLOW	3.185(R)	FAST	clk_BUFGP	0.000
R<1>	0.765(R)	SLOW	3.125(R)	FAST	clk_BUFGP	0.000
R<2>	0.762(R)	SLOW	3.119(R)	FAST	clk_BUFGP	0.000
R<3>	0.743(R)	SLOW	3.119(R)	FAST	clk_BUFGP	0.000
R<4>	0.505(R)	SLOW	3.057(R)	FAST	clk_BUFGP	0.000
R<5>	0.626(R)	SLOW	3.079(R)	FAST	clk_BUFGP	0.000
R<6>	0.773(R)	SLOW	3.113(R)	FAST	clk_BUFGP	0.000
R<7>	0.883(R)	SLOW	3.159(R)	FAST	clk_BUFGP	0.000
R<8>	0.649(R)	SLOW	3.079(R)	FAST	clk_BUFGP	0.000
R<9>	0.678(R)	SLOW	3.082(R)	FAST	clk_BUFGP	0.000
R<10>	0.817(R)	SLOW	3.118(R)	FAST	clk_BUFGP	0.000
R<11>	0.875(R)	SLOW	3.167(R)	FAST	clk_BUFGP	0.000
R<12>	0.664(R)	SLOW	3.083(R)	FAST	clk_BUFGP	0.000
R<13>	0.689(R)	SLOW	3.082(R)	FAST	clk_BUFGP	0.000
R<14>	0.813(R)	SLOW	3.112(R)	FAST	clk_BUFGP	0.000
R<15>	0.889(R)	SLOW	3.179(R)	FAST	clk_BUFGP	0.000

clk | 4.052 | 5.010 | 7.394 |

Analysis completed Mon Oct 31 13:54:39 2022

Trace Settings:

Trace Settings

Peak Memory Usage: 752 MB

## Conclusions

In conclusion, we successfully implemented a Divider on Digilent's NEXYS-4 FPGA board using an Algorithmic State Machine. We did this by utilizing datapath and control unit design

techniques to encode the algorithmic divider with the Xilinx ISE tools. This allowed us to solidify our understanding of ASMs and their underlying mechanics and logic.

### **References**


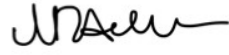
[1]: Nexys4™ FPGA Board Reference Manual, Nexys-4 rev. B; Revised November 19, 2013 by Diligent Beyond Theory

[2]: Introduction to FPGA ECE414 - Fall 2020 pdf by Randil Gajasinghe and Prof. Onur Tigli


[3]: ECE 414 Computer Organization and Design - Experiment 2. Adder/Subtractor with 7-Segment Display

[4]: Brown, S., Vranesic, Z., “Fundamentals of Digital Logic with VHDL Design,” McGraw Hill, 2000.

(-1) for turning in late report.

Rainier Young	SEU-SEG Schematics	
Brandon Rubio	Divider controller	Brandon Rubio
Nikem Dunkley-Ahmed	data path report	
Isabela Bandrich	Divider Code	Isabela Bandrich

### Lab Demonstration

Teaching Assistant Signature	Date
	28-10-22
Comments: Demonstration shown on time. Divider working.	