

**University of Miami**  
**EEN 414 Computer Organization and Design**  
**EXPERIMENT #3. Stopwatch**

**Submitted by:** Brandon Rubio, Isabela Bandrich, Rainier Young, Nikeem Dunkelly-Allen

**On:** 10/10/22

**to :** Dr. Onur Tigli

**Objective**

For this lab, we must design and verify the correct operation of a digital stopwatch using mixed modeling techniques in Verilog. Coding, verification, simulation, synthesis and timing analysis will be carried out using Xilinx ISE tools. Verified designs will be implemented on Digilent's NEXSYS4 FPGA board to show that the operation is working correctly. The Stopwatch should showcase minutes, seconds, and 1/10 seconds for a maximum of ten minutes. It should have a reset button as well as a start/pause button.

**Verilog HDL and Testbench Code**

**MAIN CODE:**

**Counter:**

```
21 module Counter(  
22     input clk,  
23     input reset,  
24     input [3:0] num,  
25     output [3:0] counter  
26 );  
27     reg [3:0] c;  
28  
29     always @(posedge clk or posedge reset)  
30     begin  
31         if(reset)  
32             c <= 4'b0000;  
33         else if(c==num)  
34             c <= 4'b0000;  
35         else  
36             c <= c + 4'b0001;  
37     end  
38  
39     assign counter = c;  
40  
41 endmodule
```

## Time Counter:

```
21 module Time_Counter(  
22     input clk,  
23     input reset,  
24     input pause,  
25     output [3:0] num_1,  
26     output [3:0] num_2,  
27     output [3:0] num_3,  
28     output [3:0] num_4  
29 );  
30 wire [3:0] out;  
31 wire [2:0] minute = 2'b10;  
32 wire [3:0] second = 3'b100;  
33 wire [17:0] ten_second = 18'd250000;  
34 wire [3:0] double_sec = 4'b0101;  
35 wire [3:0] single_sec = 4'b1001;  
36  
37 Time_Location #(18) b4(clk, reset, pause, ten_second, single_sec, out[0], num_4);  
38 Time_Location #(4) b3(out[0], reset, pause, second, single_sec, out[1], num_3);  
39 Time_Location #(4) b2(out[1], reset, pause, second, double_sec, out[2], num_2);  
40 Time_Location #(3) b1(out[2], reset, pause, minute, single_sec, out[3], num_1);  
41  
42 endmodule
```

## Clock:

```
21 module Clock(  
22     input clk,  
23     input reset,  
24     input pause,  
25     input [nBit-1:0] limit,  
26     output reg out  
27 );  
28 parameter nBit = 18;  
29 reg [nBit-1:0] counter;  
30  
31 always @(posedge clk or posedge reset or posedge pause)  
32 begin  
33     if(reset)  
34     begin  
35         counter <= 1'b0;  
36         out <= 1'b1;  
37     end  
38     else  
39     begin  
40         if(pause)  
41             counter <= counter;  
42         else  
43         begin  
44             if(counter==limit)  
45             begin  
46                 counter <= 1'b0;  
47                 out <= ~out;  
48             end  
49             else  
50             begin  
51                 counter <= counter + 1'b1;  
52                 out <= out;  
53             end  
54         end  
55     end  
56 end  
57  
58 endmodule
```

### Time Location:

```
21 module Time_Location(  
22     input clk,  
23     input reset,  
24     input pause,  
25     input [nBit-1:0] limit,  
26     input [3:0] stop,  
27     output next,  
28     output [3:0] num  
29 );  
30 parameter nBit = 18;  
31 wire count;  
32  
33 Clock #(nBit) place(clk, reset, pause, limit, count);  
34 Counter increment(count, reset, stop, num);  
35 assign next = count;  
36  
37 endmodule
```

### Seven Segment Decoder:

```
21 module Sev_Seg_Decoder(  
22     input [3:0] num_in,  
23     output [7:1] sev_seg_leds  
24 );  
25 reg [7:1] tmp;  
26 always @(*)  
27 begin  
28     case(num_in)  
29         4'h0: tmp = 7'b1000000;  
30         4'h1: tmp = 7'b1111001;  
31         4'h2: tmp = 7'b0100100;  
32         4'h3: tmp = 7'b0110000;  
33         4'h4: tmp = 7'b0011001;  
34         4'h5: tmp = 7'b0010010;  
35         4'h6: tmp = 7'b0000010;  
36         4'h7: tmp = 7'b1111000;  
37         4'h8: tmp = 7'b0000000;  
38         4'h9: tmp = 7'b0010000;  
39         default: tmp = 7'b0111111;  
40     endcase  
41 end  
42  
43 assign sev_seg_leds[7:1] = tmp;  
44  
45 endmodule
```

### Seven Segment Display with Clock:

```

21 module sev_seg_with_clk(
22     input [3:0] num_1,
23     input [3:0] num_2,
24     input [3:0] num_3,
25     input [3:0] num_4,
26     input clk,
27     input reset,
28     output [7:1] sev_seg_leds,
29     output[3:0] led_disable,
30     output reg [3:0] led_enable
31 );
32     reg [2:0] sel;
33     reg [3:0] bus;
34     assign led_disable = 4'b1111;

36     always @ (posedge clk or posedge reset)
37     begin
38         if (reset)
39             begin
40                 sel = 3'b000;
41                 led_enable = 4'b1111;
42             end
43         else
44             begin
45                 sel[2] = sel[1] & sel[0];
46                 sel[1] = sel[1] ^ sel[0];
47                 sel[0] = ~sel[0];
48                 if (sel==3'b001)
49                     begin
50                         led_enable = 4'b0111;
51                         bus = num_1;
52                     end
53                 else if (sel==3'b010)
54                     begin
55                         led_enable = 4'b1011;
56                         bus = num_2;
57                     end
58                 else if (sel==3'b011)
59                     begin
60                         led_enable = 4'b1101;
61                         bus = num_3;
62                     end
63                 else if (sel==3'b100)
64                     begin
65                         led_enable = 4'b1110;
66                         bus = num_4;
67                     end
68                 end
69             end
70
71     Sev_Seg_Decoder dec1(bus, sev_seg_leds);
72
73 endmodule

```

### Clock Stop:

```
21 module Stop_Clock(  
22     input clk,  
23     input reset,  
24     input pause,  
25     output reg out  
26 );  
27 parameter nBit = 18;  
28 reg [nBit-1:0] counter;  
29  
30 always @(posedge clk or posedge reset)  
31 begin  
32     if(reset)  
33     begin  
34         counter <= 1'b0;  
35         out <= 1'b1;  
36     end  
37     else  
38     begin  
39         if(pause)  
40         begin  
41             end  
42             else  
43                 counter <= counter;  
44         end  
45     end  
46 end  
47 endmodule
```

### Seven Segment Display with Clock - Top Module:

```

21 module sev_seg_with_clk_top(
22     input clk_main,
23     input reset,
24     input pause,
25     output [7:1] sev_seg_leds,
26     output [3:0] led_disable,
27     output reg [3:0] led_enable
28 );
29 wire [3:0] num_1;
30 wire [3:0] num_2;
31 wire [3:0] num_3;
32 wire [3:0] num_4;
33 wire clk_slw;
34 wire clk_stop;
35 wire [3:0] display;
36 reg [14:0] clk_div;
37
38 Time_Counter counter(clk_slw, reset, pause, num_1, num_2, num_3, num_4);
39 Stop_Clock hold(clk_slw, reset, pause, clk_stop);
40
41 always @(*)
42 begin
43     if(pause==1)
44         led_enable = clk_stop?4'b1111:display;
45     else
46         led_enable = display;
47 end
48
49 sev_seg_with_clk dd(num_1, num_2, num_3, num_4, clk_div[14], reset, sev_seg_leds, led_disable, display);
50 ip_clk_div clk_5M(clk_main, clk_slw);
51
52 always @(posedge clk_slw)
53 begin
54     if(reset)
55         clk_div <= 15'd0;
56     else
57         clk_div <= clk_div + 15'd1;
58 end
59
60 endmodule

```

**TESTBENCH:**

```

25 module tb_StopWatch;
26
27     // Inputs
28     reg clk;
29     reg reset;
30     reg pause;
31
32     // Outputs
33     wire [3:0] num_1;
34     wire [3:0] num_2;
35     wire [3:0] num_3;
36     wire [3:0] num_4;
37
38     // Instantiate the Unit Under Test (UUT)
39     Time_Counter uut (
40         .clk(clk),
41         .reset(reset),
42         .pause(pause),
43         .num_1(num_1),
44         .num_2(num_2),
45         .num_3(num_3),
46         .num_4(num_4)
47     );
48     integer i, j, k;
49
50     initial begin
51         // Initialize Inputs
52         clk = 0;
53         reset = 0;
54         pause = 0;
55         #10;
56
57         clk = 0;
58         reset = 1;
59         pause = 0;
60         #10;
61
62         clk = 0;
63         reset = 0;
64         pause = 0;
65         #10;

```

```

67     for(i=0;i<31'd500000000;i=i+1)
68     begin
69         clk = 0;
70         #1;
71         clk = 1;
72         #1;
73     end
74
75     clk = 1;
76     reset = 0;
77     pause = 0;
78     #10;
79
80     for(i=0;i<31'd500000;i=i+1)
81         #1 clk = ~clk;
82
83     clk = 0;
84     reset = 0;
85     pause = 0;
86     #100;
87
88     for(j=0;j<31'd2500;j=j+1)
89         #1 clk = ~clk;
90
91     clk = 0;
92     reset = 0;
93     pause = 1;
94     #100;
95
96     for(k=0;k<31'd2500;k=k+1)
97         #1 clk = ~clk;
98 end
99
100 endmodule

```


## Simulation Results

(Reset high forces counter to 0)



Name	Value	0 ns	5 ns	10 ns	15 ns	20 ns
num_1[3]:	0000	XXXX			0000	
num_2[3]:	0000	XXXX			0000	
num_3[3]:	0000	XXXX			0000	
num_4[3]:	0000	XXXX			0000	
clk	0					
reset	1					
pause	0					

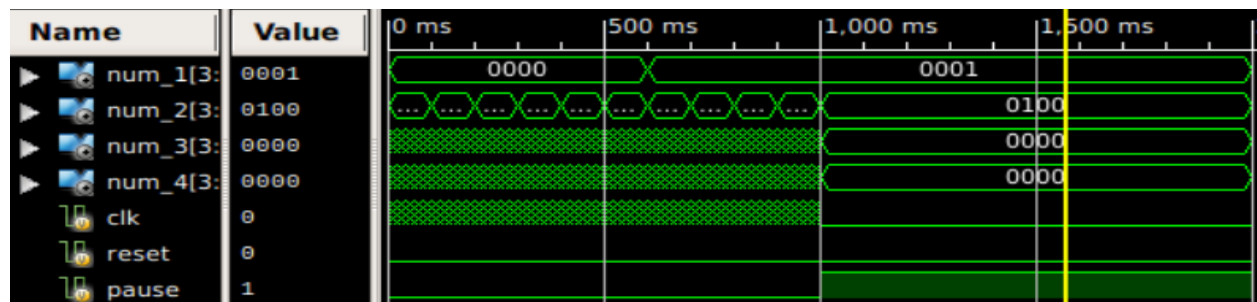(Pause high forces counter to pause/become constant)





(Normal Counting)

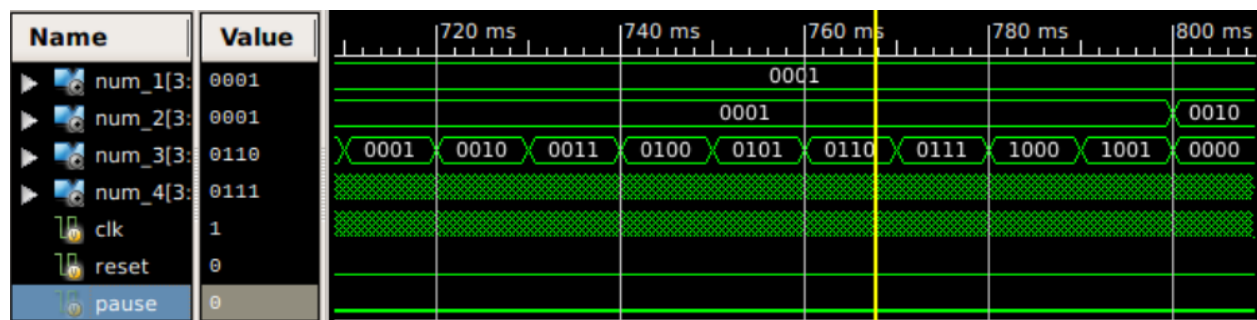 


### Pad2pad timing constraints

Met	Constraint	Check	Worst Case Slack	Best Case Achievable	Timing Errors	Timing Score
1 Yes	TS_pad2pad = MAXDELAY FROM TIMEGRP "inputs" TO TIMEGRP "o...	MAXDE...	6.933ns	13.067ns	0	0



### Device Utilization Summary

Seven Segment Display:




Device Utilization Summary				
Slice Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Registers	132	126,800	1%	
Number used as Flip Flops	103			
Number used as Latches	29			
Number used as Latch-thrus	0			
Number used as AND/OR logics	0			
Number of Slice LUTs	139	63,400	1%	
Number used as logic	138	63,400	1%	
Number using O6 output only	63			
Number using O5 output only	13			
Number using O5 and O6	62			
Number used as ROM	0			
Number used as Memory	0	19,000	0%	
Number used exclusively as route-thrus	1			
Number with same-slice register load	0			
Number with same-slice carry load	1			
Number with other load	0			
Number of occupied Slices	113	15,850	1%	
Number of LUT Flip Flop pairs used	192			
Number with an unused Flip Flop	66	192	34%	
Number with an unused LUT	53	192	27%	
Number of fully used LUT-FF pairs	73	192	38%	
Number of unique control sets	94			
Number of slice register sites lost to control set restrictions	628	126,800	1%	
Number of bonded <a href="#">IOBs</a>	18	210	8%	
Number of LOCed IOBs	18	18	100%	
Number of RAMB36E1/FIFO36E1s	0	135	0%	
Number of RAMB18E1/FIFO18E1s	0	270	0%	
Number of BUFG/BUFGCTRLs	2	32	6%	
Number used as BUFGs	2			
Number used as BUFGCTRLs	0			
Number of IDELAYE2/IDELAYE2_FINEDELAYS	0	300	0%	
Number of ILOGICE2/ILOGICE3/ISERDESE2s	0	300	0%	
Number of ODELAYE2/ODELAYE2_FINEDELAYS	0			
Number of OLOGICE2/OLOGICE3/OSERDESE2s	0	300	0%	
Number of PHASER_IN/PHASER_IN_PHYs	0	24	0%	
Number of PHASER_OUT/PHASER_OUT_PHYs	0	24	0%	
Number of BSCANs	0	4	0%	
Number of BUFHCEs	0	96	0%	
Number of BUFRs	0	24	0%	
Number of CAPTUREs	0	1	0%	
Number of DNA_PORTS	0	1	0%	
Number of DSP48E1s	0	240	0%	
Number of EFUSE_USRs	0	1	0%	
Number of FRAME_ECCs	0	1	0%	
Number of IBUFDS_GTE2s	0	4	0%	
Number of ICAPs	0	2	0%	
Number of IDELAYCTRLs	0	6	0%	
Number of IN_FIFOs	0	24	0%	
Number of MMCME2_ADVs	1	6	16%	
Number of OUT_FIFOs	0	24	0%	
Number of PCIE_2_1s	0	1	0%	
Number of PHASER_REFS	0	6	0%	
Number of PHY_CONTROLS	0	6	0%	
Number of PLLE2_ADVs	0	6	0%	
Number of STARTUPs	0	1	0%	
Number of XADCs	0	1	0%	
Average Fanout of Non-Clock Nets	2.70			



## RTL Schematic and Technology Schematic

(Ip\_clk\_div)

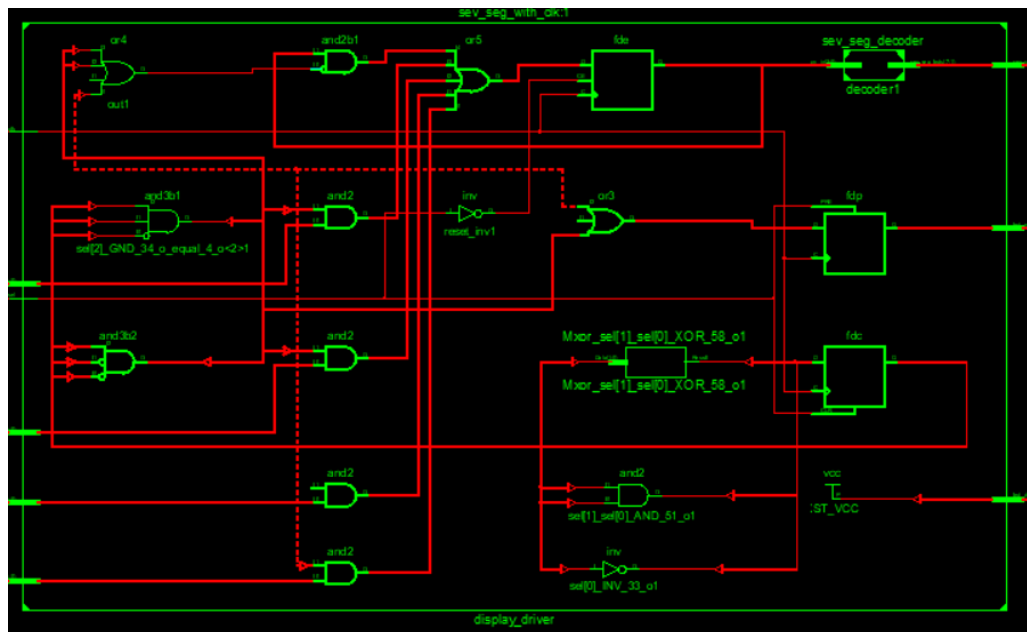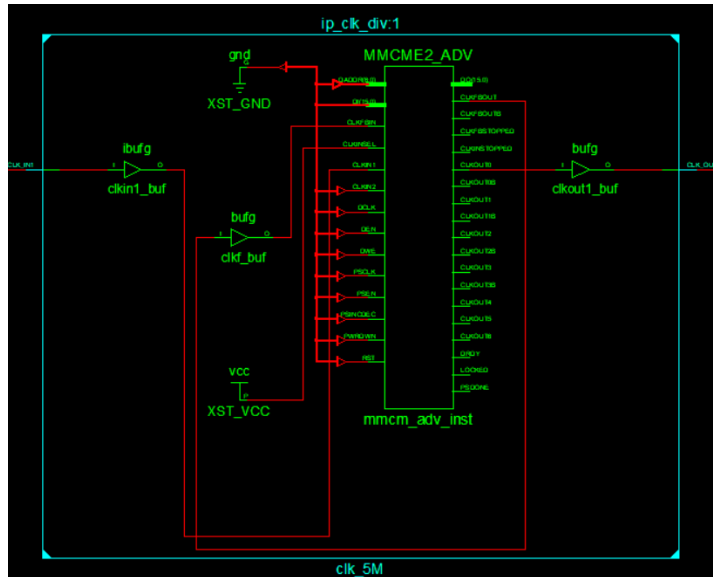


(Time Counter)

 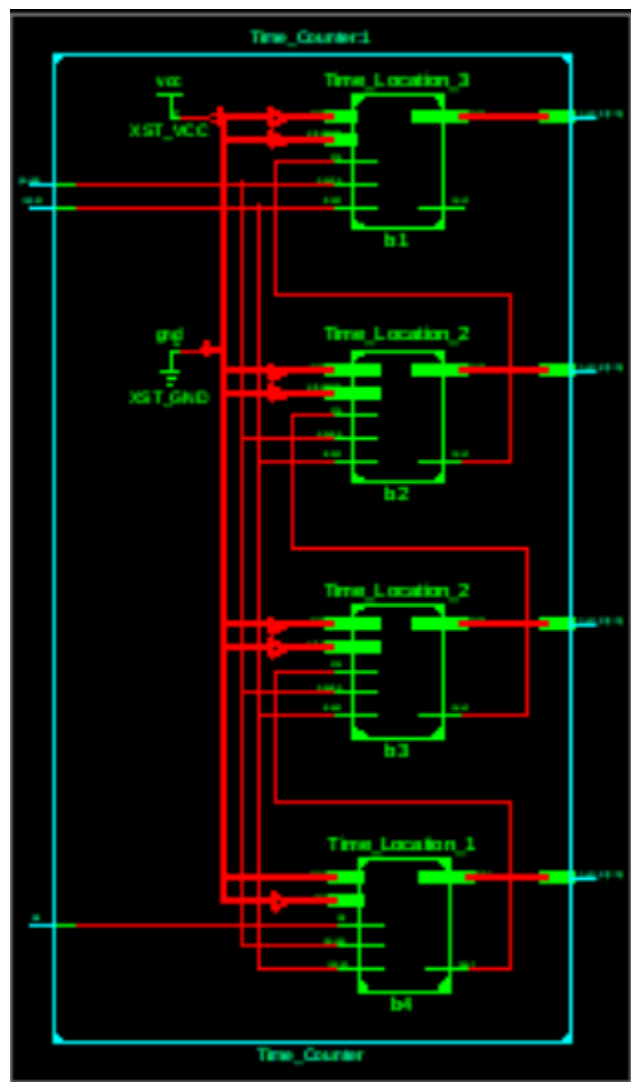 

 
 




(Seven Segment Display with Clock - Top Module)

## sev\_seg\_with\_clk\_top

 

## sev\_seg\_with\_clk\_top

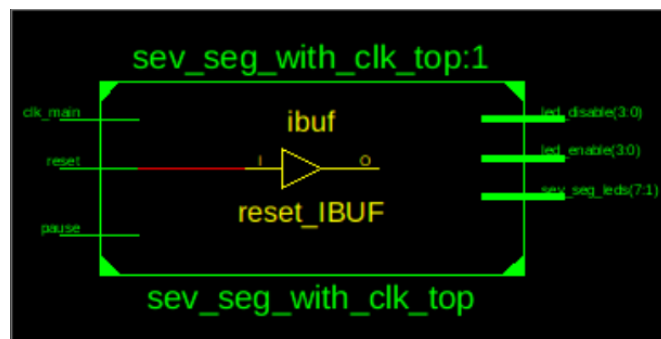 

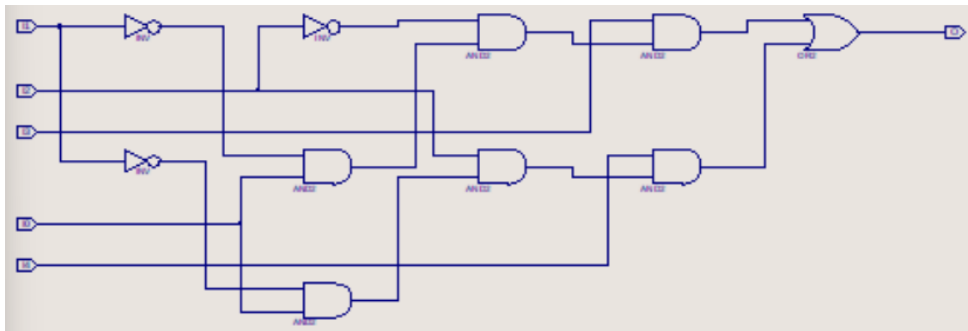 

## **Post Place and Route Static Timing**

(Seven Segment Display with Clock - Top Module)

INFO:Timing:2698 - No timing constraints found, doing default enumeration.

INFO:Timing:3412 - To improve timing, see the [Timing Closure User Guide \(UG012\)](#).

INFO:Timing:2752 - To get complete path coverage, use the unconstrained paths option. All paths that are not constrained will be reported in the unconstrained paths section(s) of the report.

INFO:Timing:3339 - The clock-to-out numbers in this timing report are based on a 50 Ohm transmission line loading model. For the details of this model, and for more information on accounting for different loading conditions, please see the device datasheet.

Data Sheet report:

-----

All values displayed in nanoseconds (ns)

Clock to Setup on destination clock clk\_main

	Src:Rise	Src:Fall	Src:Rise	Src:Fall
Source Clock	Dest:Rise	Dest:Rise	Dest:Fall	Dest:Fall
clk_main	4.442			
pause	8.815	13.553		
reset	10.874	13.553		

Clock to Setup on destination clock pause

	Src:Rise	Src:Fall	Src:Rise	Src:Fall
Source Clock	Dest:Rise	Dest:Rise	Dest:Fall	Dest:Fall
clk_main			-1.236	
pause			1.269	2.744
reset			3.438	3.438

Clock to Setup on destination clock reset

	Src:Rise	Src:Fall	Src:Rise	Src:Fall
Source Clock	Dest:Rise	Dest:Rise	Dest:Fall	Dest:Fall
clk_main			-1.236	
pause			1.362	2.744
reset			1.464	2.744

Pad to Pad

Source Pad	Destination Pad	Delay
pause	led_enable<8>	8.188
pause	led_enable<1>	7.719
pause	led_enable<2>	8.627
pause	led_enable<3>	7.791

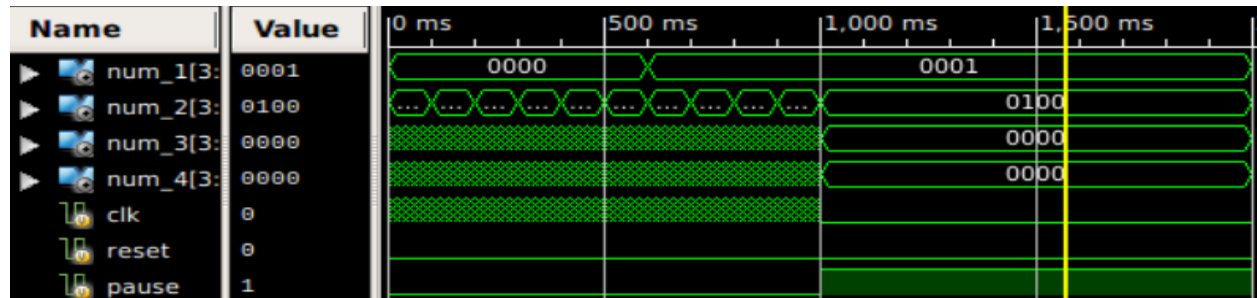
## Post Place and Route Simulation Results

(Reset high forces counter to 0)







(Pause high forces counter to pause/become constant)



(Normal Counting)

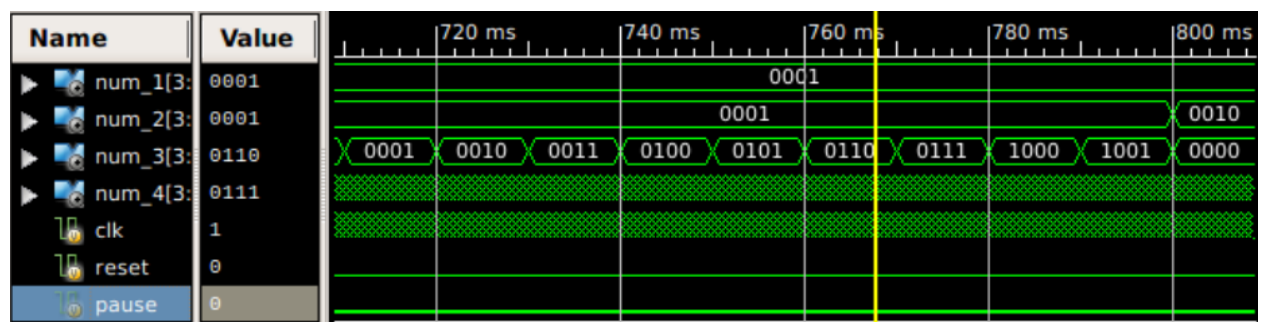 

Power Data

A	B	C	D	E	F	G	H	I	J	K	L	M	N
Device		On-Chip	Power (W)	Used	Available	Utilization (%)			Supply	Summary	Total	Dynamic	Quiescent
Family	Artix7	Clocks	0.000	35	---	---			Source	Voltage	Current (A)	Current (A)	Current (A)
Part	xc7a100t	Logic	0.000	139	63400	0			Vccint	1.000	0.018	0.001	0.017
Package	csg324	Signals	0.000	262	---	---			Vccaux	1.800	0.046	0.004	0.042
Temp Grade	Commercial	MMCMs	0.059	1	6	17			Vcco33	3.300	0.011	0.007	0.004
Process	Typical	I/Os	0.026	18	210	9			Vccbram	1.000	0.000	0.000	0.000
Speed Grade	-1	Leakage	0.088						Vccadc	1.710	0.020	0.000	0.020
		Total	0.174										
Environment													
Ambient Temp (C)	25.0												
Use custom TJA?	No												
Custom TJA (C/W)	NA												
Airflow (LFM)	250												
Heat Sink	Medium Profile												
Custom TSA (C/W)	NA												
Board Selection	Medium (10"x10")												
# of Board Layers	12 to 15												
Custom TJB (C/W)	NA												
Board Temperature (C)	NA												
Characterization													
Production	v1.0,2012-07-11												

Thermal Properties	Effective TJA (C/W)	Max Ambient (C)	Junction Temp (C)
	4.6	84.2	25.8

Supply Power (W)	Total	Dynamic	Quiescent
	0.174	0.033	0.140

## Conclusions

In this lab we utilized a 5 MHz clock to drive a modulo counter and decoded those values for display on 7 segments with the Nexys 4 FPGA board. The biggest challenge in this lab was reconfiguring the given seven segment display code from lab 2 to work in this different case. The top level design needed to be changed to display on additional displays as well as to include a counter for driving the displayed values.

## References

- [1]: Nexys4™ FPGA Board Reference Manual, Nexys-4 rev. B; Revised November 19, 2013 by Diligent Beyond Theory
- [2]: Introduction to FPGA ECE414 - Fall 2020 pdf by Randil Gajasinghe and Prof. Onur Tigli
- [3]: ECE 414 Computer Organization and Design - Experiment 2. Adder/Subtractor with 7-Segment Display